

*TMS320 DSP  
DESIGNER'S NOTEBOOK*

# ***Designing with TMS320C40 Comm Ports: Part 1***

---

---

---

*APPLICATION BRIEF: SPRA213*

*Keith Larson and Jim Patterson  
Digital Signal Processing Products  
Semiconductor Group*

*Texas Instruments  
February 1993*



## **IMPORTANT NOTICE**

Texas Instruments (TI) reserves the right to make changes to its products or to discontinue any semiconductor product or service without notice, and advises its customers to obtain the latest version of relevant information to verify, before placing orders, that the information being relied on is current.

TI warrants performance of its semiconductor products and related software to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Certain application using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS.

Inclusion of TI products in such applications is understood to be fully at the risk of the customer. Use of TI products in such applications requires the written approval of an appropriate TI officer. Questions concerning potential risk applications should be directed to TI through a local SC sales office.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards should be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or services described herein. Nor does TI warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used.

## **TRADEMARKS**

TI is a trademark of Texas Instruments Incorporated.

Other brands and names are the property of their respective owners.

### **CONTACT INFORMATION**

US TMS320 HOTLINE	(281) 274-2320
US TMS320 FAX	(281) 274-2324
US TMS320 BBS	(281) 274-2323
US TMS320 email	dsph@ti.com

## **Contents**

<b>Abstract.....</b>	<b>7</b>
<b>Design Problem .....</b>	<b>8</b>
<b>Solution .....</b>	<b>8</b>

## **Figures**

<b>Figure 1. Series Resistor Diagram .....</b>	<b>9</b>
<b>Figure 2. Example Circuit.....</b>	<b>10</b>
<b>Figure 3. Example Circuit.....</b>	<b>11</b>

# Designing with TMS320C40 Comm Ports: Part 1



## Abstract

The TMS320C40 communication port is a very-high-speed data transmission circuit. Its speed and the close proximity of multiple data lines create special challenges. The information in this document is intended to help you past some of the potential problem areas. It discusses some design issues, and gives tips to use when designing with TMS320C40 communication ports. Several schematic diagrams are given. This document has numerous references to the TMS320C40 User's Guide.



## Design Problem

What are some design issues/tips when designing with TMS320C40 communication ports?

## Solution

The TMS320C40 communication port is a very-high-speed data transmission circuit. Its speed and the close proximity of multiple data lines create special challenges. The following caveats are intended to help you past some of the potential problem areas.

First a question and answer. In the TMS320C40 User's Guide (pp. 14-33–14-35), it says that CSTRB is an output before CREQ goes high, but it also says CSTRB is an input after CREQ goes high. The timing data implies that two outputs are connected together for 0.5 clock periods. The answer is that while both TMS320C40s are driving these lines for a period of time, they are both driving in the same direction ( $V_{oh}$ ). As a result, there is no current from one device to the other.

### Signal Quality

The transmission line aspects of the communication port circuit make it sensitive to signal quality. General design rules that would be applicable to high-speed (<10 ns) memory interface design would be appropriate for TMS320C40 communication port interconnections.

Further points to keep in mind include:


- 1) An overlap feature is built into CREQ, CSTRB, and CRDY when a token is transferred. This overlap will cause these signals to all drive high (at both ends), ensuring that neither end is susceptible to floating or low-noise signals. It is important to match the clocks or else the original driver may not give up his end soon enough, which causes bus contention.
- 2) When the token exchange occurs, the falling edge of CACK indicates that there are no transfers in progress, so it is ok to drive both ends of CSTRB high (1) Figure 14-23.
- 3) The requester then acknowledges the receipt of CACK low by driving CREQ high and staying active high (3) Figure 14-23.
- 4) CREQ going high is interesting because of (5) Figure 14-24. In this case, the rising edge of CREQ causes the CREQ input to switch over to an active output high. At this time, both devices are driving CREQ high. The rising edge of CREQ also causes CACK and CSTRB to change to inputs, also with only a couple of gate delays.

- 5) Finally CACK, which is now floating, is driven active high (4) Figure 14-23. VERY IMPORTANT
- 6) The clocks of the two TMS320C40's connected together must be within a 2:1 ratio. If this is not adhered to, the overlap will last too long and the new master (the one with the faster clock) may start driving low before the old master has relinquished that line. This will cause signal contention and possibly a lot of current.

#### Design Hints

- Use series resistors in all lines. This helps match the output buffer impedance to the line impedance, protects against signal contention, and has low power dissipation. If the line length is small (6"), a single resistor in the middle can be used. The resistor value, plus buffer output impedance, should match the line impedance. The buffer output impedance is in the range of 20 to 70 ohms. A resistor value of 27 – 33 ohms may be a reasonable start. Some experimentation may be needed.

Figure 1. Series Resistor Diagram

 


- Try to keep the line impedance as high as possible. Routing signals on a top layer without a shield above them will help yield both clean signals and high impedance. Do not route signals on top of each other. When it is necessary to cross traces on adjacent layers, they should cross as right angles to reduce coupling. High line impedance will reduce the sensitivity of the circuit to changes in the output buffer impedance, and will be a benefit when interfacing to external cables, as typical ribbon cable is about 100 ohms.
- Because it is sometimes difficult to route high-impedance lines (especially long ones) in a circuit board, an external ribbon cable can be used to jump over the length of the board. In this case, only two headers need to be installed in the circuit board. Use an alternating signal and ground scheme. For quality signals a (4



control + 8 data + 1 shield)  $\times 2 = 26$ -wire ribbon is needed. The shield is needed for the signal that is otherwise on the edge.

- The driver output consists of three transistors, one pullup to  $V_{CC}$  and two pulldowns. The  $DV_{SS}$  transistor (Q2) is on above 1.8 volts and the  $CV_{SS}$  transistor (Q3) below. The advantage of a two-transistor pulldown is twofold. First, a major portion of the switching noise in Q2 is dumped into  $DV_{SS}$  and does not corrupt the clean logic  $CV_{SS}$ . Second, the ratio of Q2/Q3 and the 1.8-V switching threshold provides a nearly ideal driving signal for a wide range of transmission line impedances. Note the  $R_{on}$  values. They are quite low, and if a fault occurs something will get HOT!
- If long lengths are needed or jumps to other boards are needed, then a unidirectional data flow should be considered, as there is currently no preferred method of buffering the token for bidirectional buffers. The best method is to use slow buffers with hysteresis for CSTRB and CRDY. This has two advantages. It cleans up the signals and helps eliminate glitches, which can be erroneously perceived as valid control. It also allows the data bits to settle before the receiver sees CSTRB.


Figure 2. Example Circuit

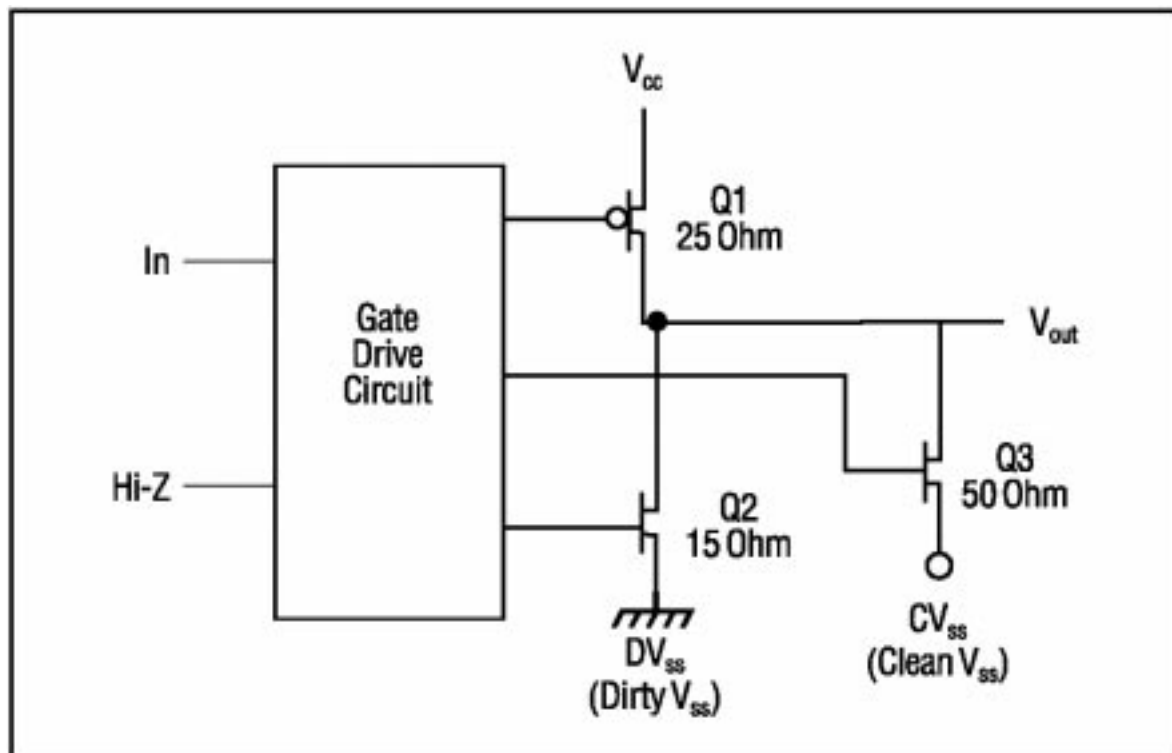

# NOTE:

The width of CSTRB low should not exceed 1.0 H at the receiving end. If it does, the byte sequencer, which has looped back to byte zero, will see this low and recognize CSTRB as the next valid byte. This is not a problem unless you are working with very long distances. In this case, use flip-flops to locally shorten CSTRB at the receiver while returning a valid CRDY width to the sender. Wide widths at the sender are not a problem. See Figure 3 for an example.

Figure 3. Example Circuit

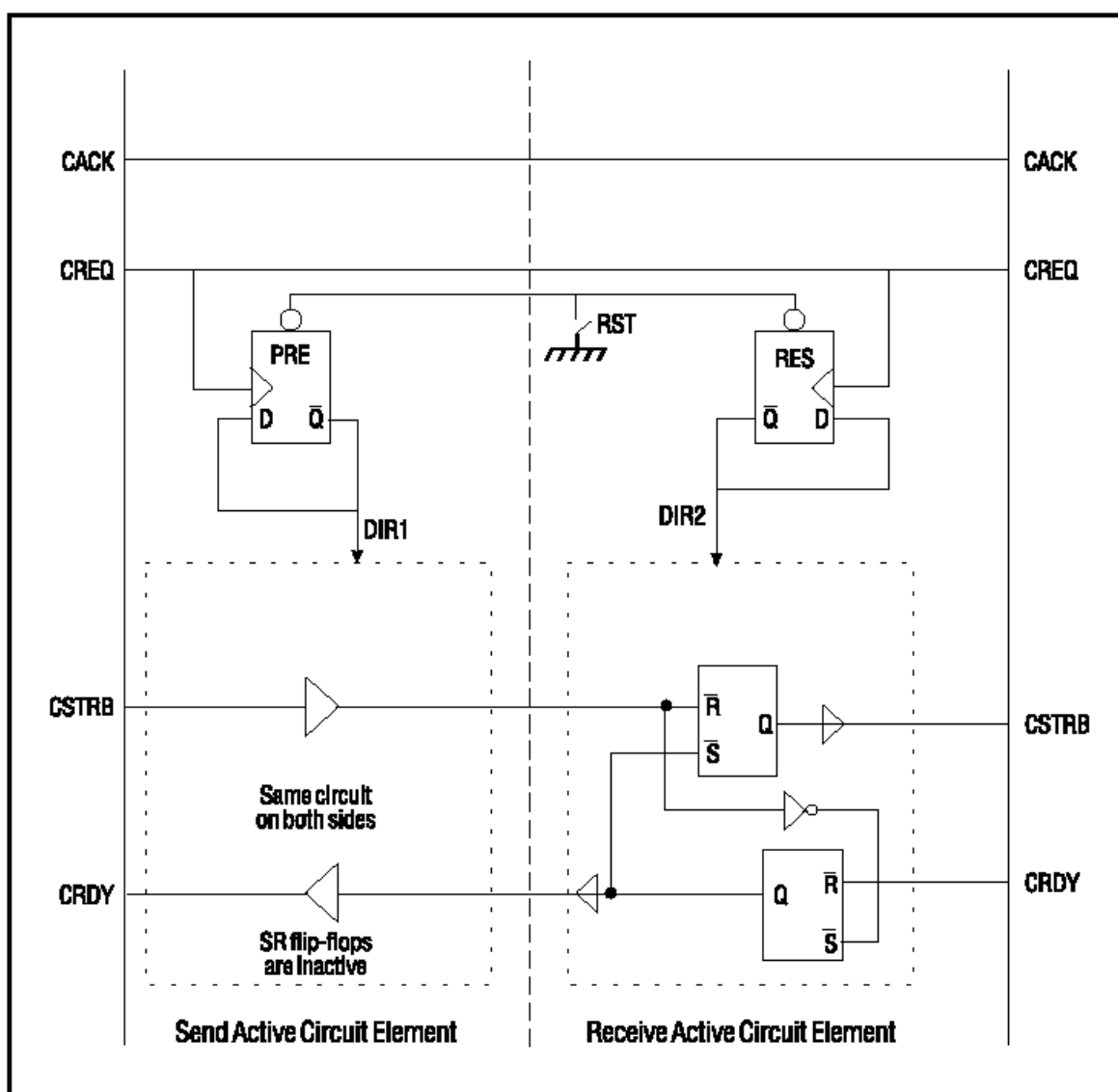



### **CSTRB Circuit With Token Direction Detection**

Because all signals are bidirectional, it is difficult to determine the direction of data transfer. A method that has been shown to work is given in Figure 3. In this case, the rising edge of CREQ is used to toggle the previous value in a flip-flop giving direction. The initial state is determined by reset at power up. Once direction is known, controlling the width of CSTRB is straightforward. Looking at the circuit you will notice that in one direction only CSTRB/CRDY buffering is done at one end and a pair of SR flips are in the circuit at the other. For the data receive end (with SRs), a low incoming CSTRB will cause the TMS320C40's pin to go low and stay low until the TMS320C40 responds with CRDY low. When CRDY falls, the TMS320C40's CSTRB (local) will go high, satisfying the 1-H criteria. When CSTRB (incoming) goes back high, the SR flip pair is ready to receive another CSTRB.

### **Conclusion**

For distances less than 12", series resistor matching is reliable so long as the design guidelines described above are adhered to. For distances greater than 12", a unidirectional transfer has been shown to be reliable when all signals are properly buffered. The width of CSTRB is important and for very long distances may need to be controlled by external logic.