

*TMS320 DSP  
DESIGNER'S NOTEBOOK*

# ***Hardware UART for the TMS320C3x***

---

---

---

*APPLICATION BRIEF: SPRA223*

*Contributed by Lawrence Wong  
Digital Signal Processing Products  
Semiconductor Group*

*Texas Instruments  
June 1993*



## **IMPORTANT NOTICE**

Texas Instruments (TI) reserves the right to make changes to its products or to discontinue any semiconductor product or service without notice, and advises its customers to obtain the latest version of relevant information to verify, before placing orders, that the information being relied on is current.

TI warrants performance of its semiconductor products and related software to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Certain application using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS.

Inclusion of TI products in such applications is understood to be fully at the risk of the customer. Use of TI products in such applications requires the written approval of an appropriate TI officer. Questions concerning potential risk applications should be directed to TI through a local SC sales office.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards should be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or services described herein. Nor does TI warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used.

## **TRADEMARKS**

TI is a trademark of Texas Instruments Incorporated.

Other brands and names are the property of their respective owners.

### **CONTACT INFORMATION**

US TMS320 HOTLINE	(281) 274-2320
US TMS320 FAX	(281) 274-2324
US TMS320 BBS	(281) 274-2323
US TMS320 email	dsph@ti.com

## **Contents**

<b>Abstract.....</b>	<b>7</b>
<b>Design Problem .....</b>	<b>8</b>
<b>Solution .....</b>	<b>8</b>

## **Figures**

<b>Figure 1. Hardware UART .....</b>	<b>8</b>
<b>Figure 2. Transmit Circuitry .....</b>	<b>9</b>
<b>Figure 3. Receive Circuitry .....</b>	<b>10</b>

# Hardware UART for the TMS320C3x

---

---

---

## Abstract

The TMS320C3X does not offer a UART for asynchronous communication. On the TI Digital Signal Processor BBS there is a software UART emulator available. This will allow the TMS320C3x to perform asynchronous communication. There are some instances that a hardware UART may be necessary for a particular application. This document describes one possible solution for implementing a hardware UART. This design was originally done in an FPGA and it can be easily transferred to an ASIC. Modification to this design can be done to accommodate faster data rates or different communication protocols. Several schematics are provided.


## Design Problem

The TMS320C3X does not offer a UART for asynchronous communication.

## Solution


On the TI DSP BBS there is a software UART emulator available. This will allow the TMS320C3x to perform asynchronous communication. There are some instances that a hardware UART may be necessary for a particular application. The following describes one possible solution for implementing a hardware UART. This design was originally done in an FPGA and it can be easily transferred to an ASIC. Modification to this design can be done to accommodate faster data rates or different communication protocols.

Figure 1. Hardware UART

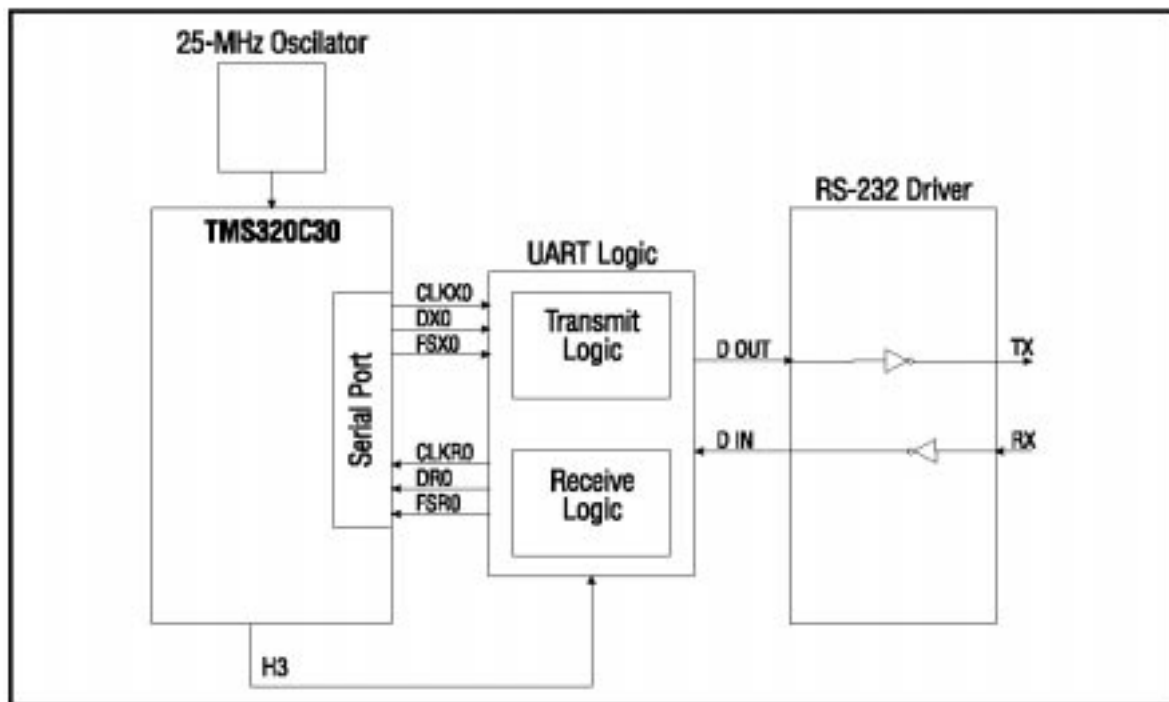

The following schematic is for a 9600-baud UART with one stop bit and a start bit. The clock signal, H3, is supplied to the circuit from the TMS320C3x. The DSP was running with a 25-MHz clock, which was necessary for a particular application. Modification to the FPGA timing circuit will be necessary to accommodate a higher clock speed for the DSP.

Figure 2. Transmit Circuitry

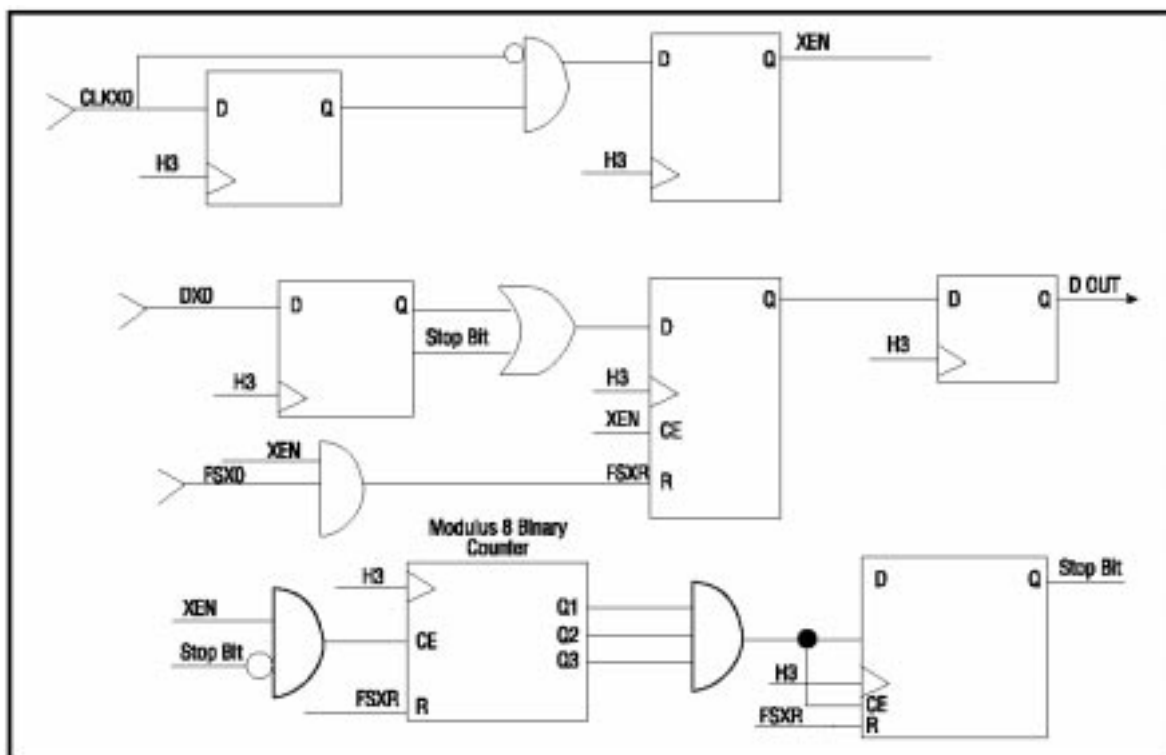

The TMS320C30 transmit section of the serial port is configured to output eight bits of data at a rate of approximately 9.6 kHz. This is achieved by using one of the TMS320C30's internal timers and programming it to the desired 9.6 kHz frequency. The transmitting port is configured in the fixed burst mode. This allows the leading FSX signals to help initiate a start bit for the UART protocols. The stop bit is generated at the end of the eighth bit by the UART circuitry.

The receive section of the UART is activated when the circuitry detects the start bit. The start bit is a logical zero. The delay circuit is activated on the falling edge of the start bit. The delay is used so that sampling of the incoming data bits occur in the middle of the signal level, thus causing the UART to have a higher noise immunity.



