

*TMS320 DSP  
DESIGNER'S NOTEBOOK*

# ***Guidelines for Using Decoupling Capacitors on DSP Designs***

---

---

---

*APPLICATION BRIEF: SPRA230*

*Ralph Weir and Gene Frantz  
Digital Signal Processing Products  
Semiconductor Group*

*Texas Instruments  
June 1993*



## **IMPORTANT NOTICE**

Texas Instruments (TI) reserves the right to make changes to its products or to discontinue any semiconductor product or service without notice, and advises its customers to obtain the latest version of relevant information to verify, before placing orders, that the information being relied on is current.

TI warrants performance of its semiconductor products and related software to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Certain application using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS.

Inclusion of TI products in such applications is understood to be fully at the risk of the customer. Use of TI products in such applications requires the written approval of an appropriate TI officer. Questions concerning potential risk applications should be directed to TI through a local SC sales office.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards should be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or services described herein. Nor does TI warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used.

## **TRADEMARKS**

TI is a trademark of Texas Instruments Incorporated.

Other brands and names are the property of their respective owners.

## **CONTACT INFORMATION**

US TMS320 HOTLINE	(281) 274-2320
US TMS320 FAX	(281) 274-2324
US TMS320 BBS	(281) 274-2323
US TMS320 email	dsph@ti.com

## Contents

Abstract.....	7
Design Problem .....	8
Solution .....	8

# Guidelines for Using Decoupling Capacitors on DSP Designs

---

---

---

## Abstract

This document provides some guidelines for selecting decoupling capacitors for TMS320C3x devices.



## Design Problem

What are some guidelines for selecting decoupling capacitors for TMS320C3x devices?

## Solution

On page 13-14 of the TMS320C3x Users Guide, there is a note that recommends using 0.1  $\mu\text{F}$  decoupling capacitors on the  $V_{\text{dd}}$  pins of the TMS320C31. Here we will provide tips on the number and types of capacitors you should use.

1) On a multilayer PCB with separate  $V_{\text{cc}}/V_{\text{dd}}$  planes, half a dozen 0.1  $\mu\text{F}$  will be ample. This assumes that other devices (e.g., memories) are decoupled adequately. Ceramics are the right choice. The real rule is to find capacitors with no inductive component. Electrolytics, for example, have a significant amount of inductance due to their manufacturing method. That is why in many switching regulators you find a large electrolytic in parallel with a small ceramic capacitor.

### NOTE:

You can use capacitors in the range of 0.01  $\mu\text{F}$  to 0.2  $\mu\text{F}$ . The purpose is to eliminate noise spikes. You may need to tune to the circuit for a specific noise component.

2) Put the holes necessary to bypass every  $V_{\text{dd}}$  pin on the board such that the capacitors can be auto attached. This not only provides the places for the capacitors, but allows for repair procedures in the future when a noise problem occurs. Don't populate all of the locations for cost reasons, but have the vacant locations there if needed. A corollary is to put the pads down for bypass capacitors on other signals that might need them. Actually, if well thought out, other components besides capacitors can be placed in these locations. For example bypass capacitors on address, data, and control lines. Later these could be used for many other things (e.g., pull-up/pull-down resistors). The simple rule is that PCBs are expensive to modify or repair.

3) If a board has DRAM on it, make sure that you have slightly more 0.1  $\mu\text{F}$  ceramics, but add a couple of bigger tantalums – e.g., 10  $\mu\text{F}$ . This is because a DRAM refresh cycle eats power and can cause the whole board's power rails to drop.

4) Make sure that the power tracks are wide, low-impedance vias.

5) If a board has problems after following these guidelines, try decoupling with additional mylar capacitors. These have a great frequency response but will add to the power consumption.