

*TMS320 DSP
DESIGNER'S NOTEBOOK*

Configuring PWM Outputs of TMS320F240 with Dead Band for Different Power Devices

APPLICATION REPORT: SPRA289

*Mohammed S Arefeen
Source Organization*

*Digital Signal Processing Solutions
November 1997*



IMPORTANT NOTICE

Texas Instruments (TI) reserves the right to make changes to its products or to discontinue any semiconductor product or service without notice, and advises its customers to obtain the latest version of relevant information to verify, before placing orders, that the information being relied on is current.

TI warrants performance of its semiconductor products and related software to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Certain application using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS.

Inclusion of TI products in such applications is understood to be fully at the risk of the customer. Use of TI products in such applications requires the written approval of an appropriate TI officer. Questions concerning potential risk applications should be directed to TI through a local SC sales office.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards should be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or services described herein. Nor does TI warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used.

TRADEMARKS

TI is a trademark of Texas Instruments Incorporated.

Other brands and names are the property of their respective owners.

CONTACT INFORMATION

US TMS320 HOTLINE	(281) 274-2320
US TMS320 FAX	(281) 274-2324
US TMS320 BBS	(281) 274-2323
US TMS320 email	dsph@ti.com

Contents

Abstract	7
Product Support.....	8
World Wide Web	8
Email.....	8
Design Problem.....	9
Solution.....	9
Example	11

Figures

Figure 1. PWM1 & PWM2 without Dead Band: PWM1 (top) Active High and PWM2 (bottom) Active Low.....	9
Figure 2. PWM1 (Active High) and PWM2 (Active Low) Outputs with Dead Band.....	10
Figure 3. PWM1 (Active Low) and PWM2 (Active High) Outputs with Dead Band.	10
Figure 4. Both PWM1 and PWM2 Configured Active High with Dead Band.	10
Figure 5. Both PWM1 and PWM2 Configured As Active Low with Dead Band.....	11
Figure 6. Inverter Phase with Two Power Devices Connected In Series.	11

Tables

Table 1. The PWM Output Configurations with Dead Band for Various Power Devices ...	12
---	----

Configuring PWM Outputs of TMS320F240 with Dead Band for Different Power Devices

Abstract

The DSP controller TMS320F240 has a programmable dead band generator, to insert a dead band between two PWM outputs. The polarity of PWM channels (active high or active low) can be controlled using the ACTR register. The appropriate dead band between two PWM outputs can be inserted using the DBTCON register. This document describes how to configure the PWM outputs with dead band for different power devices.



Product Support

World Wide Web

Our World Wide Web site at www.ti.com contains the most up to date product information, revisions, and additions. Users registering with TI&ME can build custom information pages and receive new product updates automatically via email.

Email

For technical issues or clarification on switching products, please send a detailed email to dsph@ti.com. Questions receive prompt attention and are usually answered within one business day.

Design Problem

How do I configure PWM outputs with dead band for different power devices?

Solution

The DSP controller TMS320F240 has a programmable dead band generator to insert a dead band between two PWM outputs (PWM1&2, PWM3&4, and PWM5&6). The polarity of PWM channels (active high or active low) can be controlled using the ACTR register. The appropriate dead band between two PWM outputs can be inserted using the DBTCON register. The dead band circuitry of the TMS320F240 reduces the active portion of the odd PWM channels (PWM1, PWM3, and PWM5) from the leading transition end. However, the dead band circuitry of TMS320F240 increases the active portion of the even PWM channels (PWM2, PWM4, and PWM6) from the lagging transition end. The following figures show different PWM waveform configurations with dead band. Figure 1 shows PWM1 (active high) and PWM2 (active low) without dead band. The counter is operating in continuous up/down mode and the transitions in PWM outputs occur at every compare match. The compare match event is shown by dotted lines in Figure 2 through Figure 5.

Figure 1. PWM1 & PWM2 without Dead Band: PWM1 (top) Active High and PWM2 (bottom) Active Low.

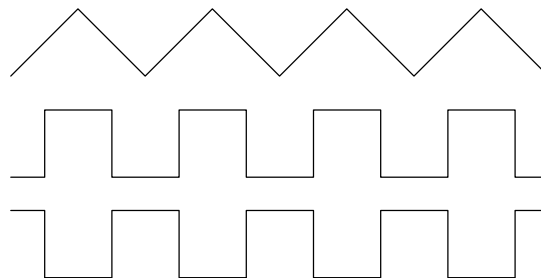


Figure 2 shows PWM1 and PWM2 configured as active high and active low respectively, with dead band.

Figure 2. PWM1 (Active High) and PWM2 (Active Low) Outputs with Dead Band.

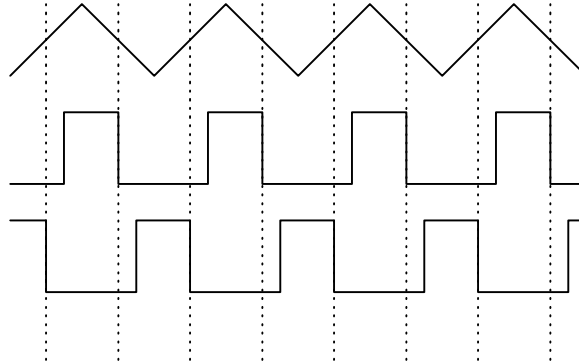


Figure 3 shows PWM1 and PWM2 configured as active low and active high respectively, with dead band.

Figure 3. PWM1 (Active Low) and PWM2 (Active High) Outputs with Dead Band.

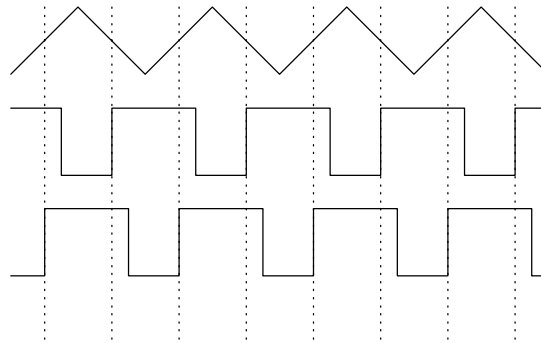


Figure 4 shows both PWM1 and PWM2 configured as active high with dead band.

Figure 4. Both PWM1 and PWM2 Configured Active High with Dead Band.


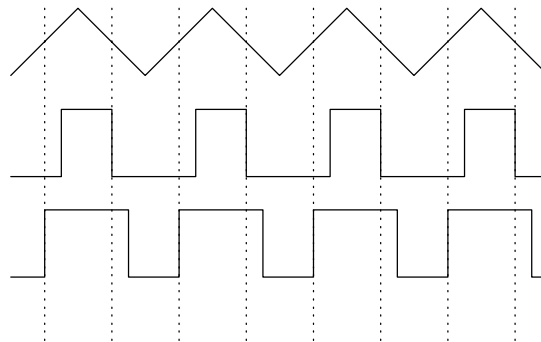


Figure 5 shows both PWM1 and PWM2 configured as active low with dead band.

Figure 5. Both PWM1 and PWM2 Configured As Active Low with Dead Band.

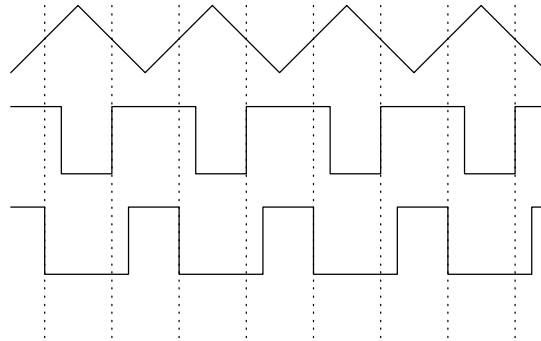


Note that in all the cases shown in Figure 2 through Figure 5, the active portion of PWM1 is reduced and the active portion of PWM2 is increased by the introduction of dead band.

Example

Figure 6 shows a phase of an inverter that needs dead band to prevent shoot through fault.

Figure 6. Inverter Phase with Two Power Devices Connected In Series.

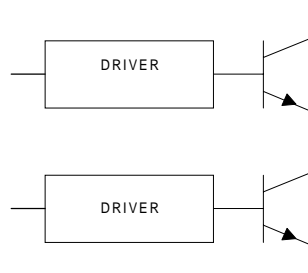

Suppose that both power devices turn on when the driver gets high voltage, and turn off when the driver gets low voltage. In this case the PWM outputs with dead band should be configured as shown in Figure 2.

If both power devices turn on with low voltage and turn off with high voltage, then the PWM outputs with dead band should be configured as shown in Figure 3.

If the upper device needs high voltage to turn on and the lower device needs low voltage to turn on, then the PWM outputs with dead band should be configured as shown in Figure 4.

If the upper device needs low voltage to turn on and the lower device needs high voltage to turn, on then the PWM outputs with dead band should be configured as shown in Figure 5.

Table 1. The PWM Output Configurations with Dead Band for Various Power Devices

Power Devices Configurations				PWM output configurations			
In order to turn ON, upper switch needs - (V)		In order to turn ON, lower switch needs - (V)		Polarity of PWMx x = 1,3, and 5		Polarity of PWMy y = 2,4, and 6	
High	Low	High	Low	Active Hi	Active Lo	Active Hi	Active Lo
X		X		X			X
	X		X		X	X	
X			X	X		X	
	X	X			X		X